

## Application: Differentiator Circuits

**Objective: To understand how the properties of the Fourier transform allow us to design a circuit that differentiates the input signal with respect to time.**

Recall the Fourier transform (ordinary frequency version):

$$\hat{f}(\xi) = \int_{-\infty}^{\infty} f(t) e^{-2\pi j \xi t} dt,$$

and its inverse transform:

$$f(t) = \int_{-\infty}^{\infty} \hat{f}(\xi) e^{2\pi j \xi t} d\xi.$$


Recall also that

$$\widehat{\frac{df}{dt}}(\xi) = (2\pi j \xi) \hat{f}(\omega).$$


The output voltage  $V_{\text{out}}$  of an op-amp (shown below) depends on the two input voltages  $V_1$  and  $V_2$  according to

$$V_{\text{out}} = G(V_1 - V_2),$$

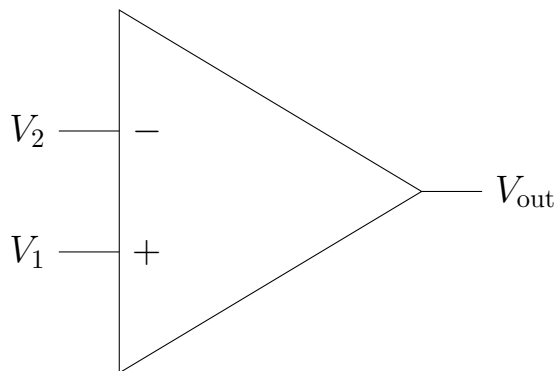where  $G$  is some very large number (the gain of the amplifier).



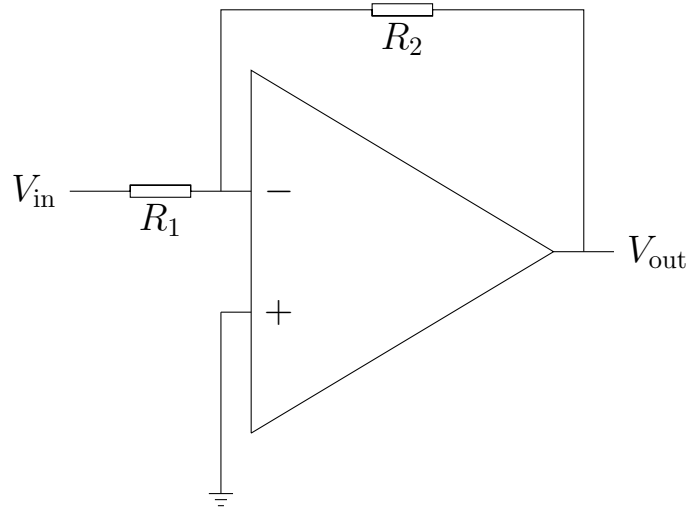Suppose we connect the output of the op-amp through a voltage divider to the negative input, as shown, and tie the positive input to ground:



We assume that the input impedance of the op-amp is extremely high, so no current flows into or out of the op-amp inputs. Let  $V_0$  denote the voltage at the negative input of the op-amp.

1. By considering current, show that

$$\frac{V_{\text{out}} - V_0}{R_2} = \frac{V_0 - V_{\text{in}}}{R_1}.$$

2. Hence show that

$$V_{\text{out}} = V_0 \left( 1 + \frac{R_2}{R_1} \right) - \frac{R_2}{R_1} V_{\text{in}}.$$


3. By considering the effect on  $V_{\text{out}}$  if  $V_0 > 0$  and if  $V_0 < 0$  respectively, show that the action of the circuit is to make  $V_0 = 0$ .

4. Hence conclude that the output of the circuit is given by

$$V_{\text{out}} = -\frac{R_2}{R_1} V_{\text{in}}.$$

5. Now suppose that  $R_1$  is replaced by a capacitor,  $C$ . Recall that the impedance of a capacitor when a sinusoidal voltage of frequency  $\xi$  is applied is given by

$$\frac{1}{2\pi\xi jC}.$$

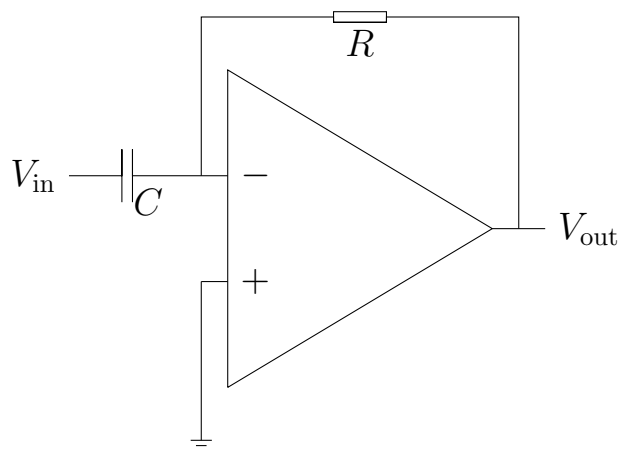

Show that if  $V_{\text{in}}$  is a sinusoid of amplitude  $A$ , then the amplitude of  $V_{\text{out}}$  is given by

$$-2\pi\xi jRC A.$$

6. Suppose that  $V_{\text{in}} = f(t)$  is some time-varying function. Show that the Fourier transform of  $V_{\text{out}}$  is given by

$$-2\pi\xi jRC \hat{f}(\omega).$$

7. Hence conclude that the (time-domain) output of the circuit is

$$V_{\text{out}}(t) = -RC \frac{dV_{\text{in}}}{dt}.$$

8. Suppose instead that we leave  $R_1$  as a resistor and replace instead  $R_2$  by the capacitor  $C$ , as shown below. Suppose the circuit is switched on at time 0, and before that has 0V input and output. By carrying out a similar frequency-domain analysis, show that the output of the circuit is now given by

$$V_{\text{out}}(t) = -\frac{1}{RC} \int_0^t V_{\text{in}}(\tau) d\tau,$$

where  $\tau$  is a dummy variable of integration.

